

The ngspice RF / periodic steady-state suite

A beginner's guided tour: PSS, HB, PAC/Pnoise/PXF/PSP, QPSS, phase noise, envelope following

Ngspice + OpenVAF Enhancements project

July 2026

Contents

The ngspice RF / periodic steady-state suite	1
Part 0 — What problem is the RF suite solving?	2
Part 1 — S-parameters (.sp)	3
Part 2 — Periodic steady state: .pss and hb	5
Part 3 — Periodic AC: conversion gain (.pac)	8
Part 4 — Periodic noise (.pnoise)	9
Part 5 — Periodic transfer function (.pxf) and S-parameters (.psp)	10
Part 6 — Two tones at once: quasi-periodic steady state (qpss)	11
Part 7 — Oscillators: hbosc + phasenoise	13
Part 8 — Envelope following (envelope)	14
Part 8b — Design aids built on the same machinery	15
Part 9 — It all works under both linear solvers	15
Summary	16

The ngspice RF / periodic steady-state suite

This document is a guided tour of the RF analysis suite that these enhancements added to ngspice: periodic steady state, harmonic balance, periodic AC / noise / transfer / S-parameters, two-tone (quasi-periodic) analyses, oscillator phase noise, and envelope following. It is written so that a reader with no prior RF-simulation background can follow along: every analysis comes with a plain-language explanation, a circuit schematic, a complete runnable netlist, the exact command, a plot of the real ngspice result, and a discussion of *why the result is physically correct*.

Every example is a real circuit you can paste into a file and run. Half of them use ngspice's built-in devices (resistors, capacitors, diodes, behavioral sources); the other half use OSDI devices — compact models written in Verilog-A and compiled to a .osdi library by `openvaf-r` — so you can see that the RF analyses treat both identically. The schematics were drawn with [schemdraw](#); the result plots were generated from real runs of the committed ngspice by [make_rf_figs.py](#), and the schematics by [make_rf_schematics.py](#).

How the enhancement links work. Each analysis links to the enhancement write-up(s) that implemented it — for example [Enhancement-117](#). The [gap analysis](#) has the bird's-eye view of the whole suite.

Part 0 — What problem is the RF suite solving?

If you have used SPICE at all, you know its three classic analyses:

Analysis	Question it answers	ngspice card
Operating point	Where does the circuit sit at rest (all DC)?	<code>.op</code>
AC	If I wiggle the input by a <i>tiny</i> sine, how does the circuit respond vs. frequency?	<code>.ac</code>
Transient	What does every voltage do over time, step by step?	<code>.tran</code>

These are enough for audio, power, and digital work. They start to hurt for radio-frequency (RF) circuits — mixers, amplifiers, oscillators, filters at MHz–GHz — for two reasons:

1. RF circuits are driven hard and periodically. A mixer is *pumped* by a large "local oscillator" tone. The circuit's response is not a tiny wiggle around a DC point (so `.ac` does not apply), but a tiny wiggle around a large, repeating waveform. You need the *periodic* operating state first, then the small-signal behaviour around it.
2. You care about the frequency domain, cheaply. A `.tran` of an oscillator settling over 10 000 cycles, or of a mixer converting a weak signal, is enormously expensive and then needs an FFT with careful windowing. RF analyses compute the steady, repeating answer *directly* — often in the frequency domain — with no long time-marching.

The RF suite adds exactly these tools. Two ideas recur throughout, so let's name them now in plain language:

- Harmonics. Push a pure sine at frequency f through anything nonlinear (a diode, a transistor) and the output contains not just f but also $2f$, $3f$, ... — *harmonics*. A "periodic steady state" is fully described by the amplitudes and phases of f and its harmonics.
- Mixing / conversion. Put *two* tones into a nonlinearity and you get sums and differences: $f_1 \pm f_2$, $2f_1 - f_2$, ... A mixer uses this on purpose (radio → audio); an amplifier suffers it as distortion. Small signals injected near a big "pump" tone get converted to new frequencies (sidebands). The periodic small-signal analyses (`.pac`, `.pnoise`, `.pxf`) are all about this conversion.

The rest of the document walks the suite roughly in order of difficulty. Here is the map:

Analysis	Command	What it computes	Enhancements
S-parameters	<code>.sp</code>	how an N-port reflects/transmits vs. frequency	63 , 64/72
Periodic steady state	<code>.pss</code>	the repeating large-signal waveform	117 , 118
Harmonic balance	<code>hb</code>	the same, solved in the frequency domain	134 , 135
Periodic AC	<code>.pac</code>	small-signal gain/conversion around a pumped state	119–123
Periodic noise	<code>.pnoise</code>	noise of a pumped circuit (incl. cyclostationary)	124 , 126
Periodic transfer fn	<code>.pxf</code>	input→output transfer through the pumped state	125
Periodic S-parameters	<code>.psp</code>	S-parameters of a pumped (time-varying) network	132


Analysis	Command	What it computes	Enhancements
Two-tone steady state	qpss	intermodulation from two independent tones	133 , 136
Two-tone small-signal	qpac/qpnoise/qpnoise	the .pac/.pnoise/.pxf trio, two-tone	137–142
Oscillator phase noise	hbosc + phasenoise	an oscillator's frequency and its noise skirt	140
Envelope following	envelope	the slow envelope of a fast carrier	154

A note on OSDI devices: several examples load a small Verilog-A model library, `rf_blocks.osdi`, that defines a resistor `ores`, a capacitor `ocap`, and a diode `odio`. You compile it once from `rf_blocks.va` with `openvaf-r rf_blocks.va` and load it in a deck with `pre_osdi rf_blocks.osdi`. Instances use an N-prefixed name and a `.model` card, e.g. `N1 in out mm +.model mm ores r=100`.

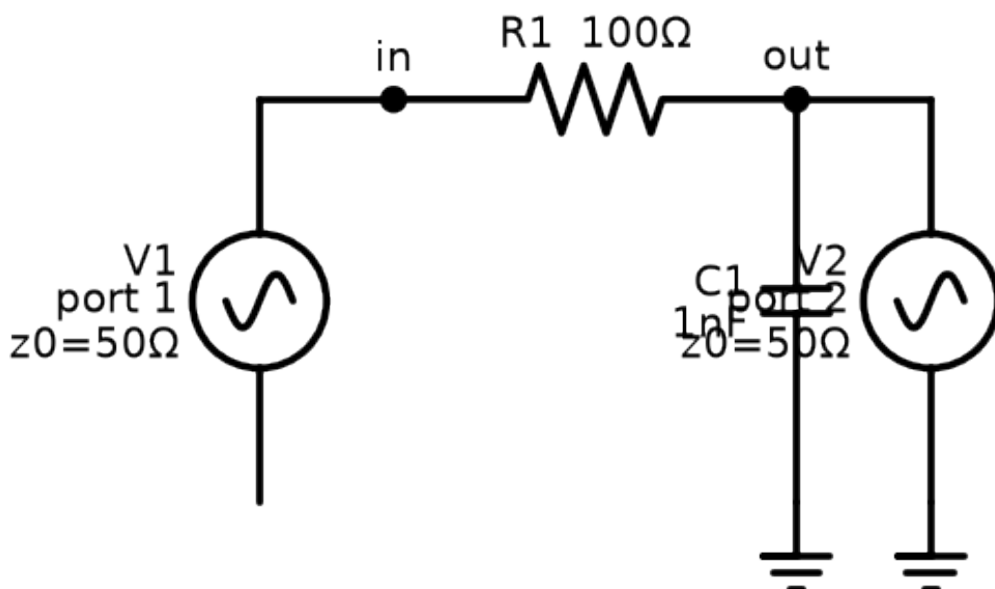Part 1 — S-parameters (`.sp`)

The idea. At high frequency we stop talking about “voltage in, voltage out” and start talking about waves. A signal travelling down a $50\text{-}\Omega$ cable that hits your circuit is partly reflected and partly transmitted. S-parameters are just the bookkeeping for those waves: `S11` is “how much bounces back off port 1” (reflection), `S21` is “how much gets through to port 2” (transmission/gain). They are complex numbers versus frequency, and they are *the* language of RF design. `.sp` was added in [Enhancement-63](#); import/export of the standard Touchstone file format in [E-64/E-72](#).

The circuit. The simplest instructive example is an RC low-pass filter sitting between a $50\text{-}\Omega$ source and a $50\text{-}\Omega$ load:



Built-in netlist. Ports are declared by adding `portnum` and `z0` (reference impedance) to voltage sources:

```
* S-parameters of an RC low-pass filter (built-in R, C)
R1 in out 100
C1 out 0 1n
V1 in 0 DC 0 AC 1 portnum 1 z0 50
V2 out 0 DC 0 AC 1 portnum 2 z0 50
.sp dec 30 100k 1g
```


```
.control
run
plot vdb(S_2_1)      $ |S21| in dB versus frequency
.endc
.end

.sp dec 30 100k 1g sweeps 30 points per decade from 100 kHz to 1 GHz.
```

OSDI netlist (same circuit, Verilog-A devices). Replace the built-in R1/C1 with OSDI ores/ocap instances — nothing else changes:

```
* S-parameters of an RC low-pass filter (OSDI Verilog-A R, C)
.control
pre_osdi rf_blocks.osdi
.endc
N1 in out mm
.model mm ores r=100
N2 out 0 mmc
.model mmc ocap cap=1n
V1 in 0 DC 0 AC 1 portnum 1 z0 50
V2 out 0 DC 0 AC 1 portnum 2 z0 50
.sp dec 30 100k 1g
.control
run
plot vdb(S_2_1)
.endc
.end
```

The result.

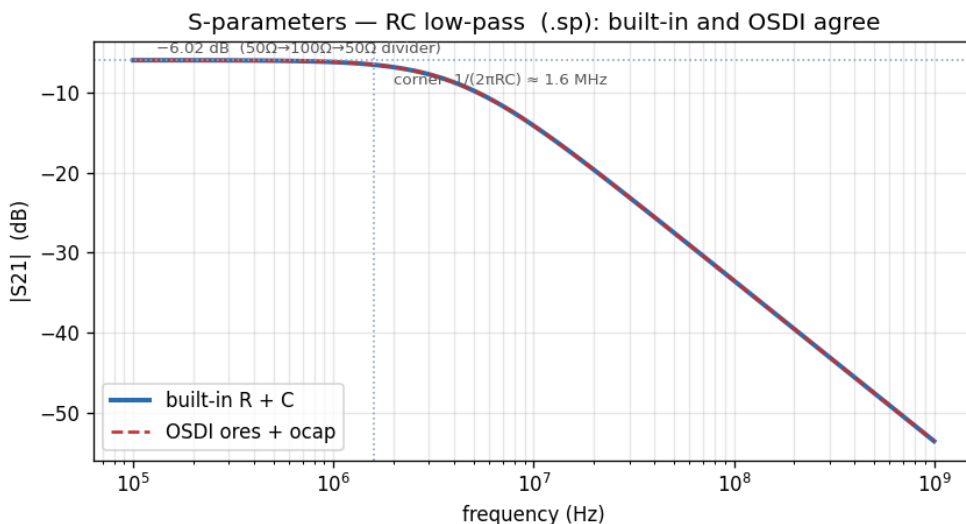

Why it is physically correct. Two features pin it down exactly:

- Low-frequency floor of -6.02 dB. At low frequency the capacitor is an open circuit, so the network is just the $100\text{-}\Omega$ series resistor between a $50\text{-}\Omega$ source and a $50\text{-}\Omega$ load. For a series resistor R between equal ports Z_0 , transmission is $S_{21} = 2 \cdot Z_0 / (2 \cdot Z_0 + R) = 100/200 = 0.5$, and $20 \cdot \log_{10}(0.5) = -6.02$ dB. The simulated curve sits exactly there.
- Roll-off above the corner. The capacitor shorts the output at high frequency; the response falls at 20 dB/decade past the corner $1/(2\pi RC) = 1/(2\pi \cdot 100 \cdot 1\text{nF}) \approx 1.6$ MHz.

The built-in and OSDI curves lie on top of each other — the S-parameter engine reads the device con-

ductance/susceptance the same way whether the device is compiled C or a Verilog-A model.

Part 2 — Periodic steady state: **.pss** and **hb**

Now we leave linear filters behind. An RF circuit driven by a large tone settles into a periodic steady state (PSS): after transients die out, every node repeats exactly every period $T = 1/f$. There are two ways to find it, and ngspice has both.

2a. Shooting PSS (**.pss**)

.pss ([Enhancement-117](#), [-118](#)) uses a shooting method: it guesses the state at $t=0$, integrates one period, and adjusts the guess until the end state matches the start — i.e. until the waveform truly repeats. It is a brute-force method: reliable and accurate on linear-to-moderately-nonlinear circuits, and the foundation the periodic small-signal analyses (**.pac**, **.pnoise**, **.pxf**, **.psp**) are built on.


```
* Periodic steady state of a driven RC (built-in)
V1 a 0 SIN(0 1 1meg)
R1 a b 1k
C1 b 0 1n
* .pss Fguess StabTime OscNode Points Harmonics SC_iter Steady_coeff
.pss 1meg 1u b 512 8 40 5u
.control
run
.endc
.end
```

The arguments read: guess the period from 1meg (1 MHz), let transients settle for 1u (1 μ s), watch node b, sample the period at 512 points, keep 8 harmonics, allow 40 shooting iterations, with a steadiness tolerance coefficient 5u. For this linear RC the periodic steady state is simply the 1 MHz sinusoid — which is the point of using it here as a gentle first run. Its real value shows up in the small-signal analyses below.

2b. Harmonic balance (**hb**)


hb ([Enhancement-134](#), [-135](#)) finds the *same* periodic steady state but works directly in the frequency domain: it represents each node as a sum of a DC term plus K harmonics, and solves for all their amplitudes/phases at once with a Newton iteration. It is robust on strongly nonlinear circuits (it has automatic source-stepping continuation), which makes it the right tool for the harmonic-generation demo the shooting method finds hard.

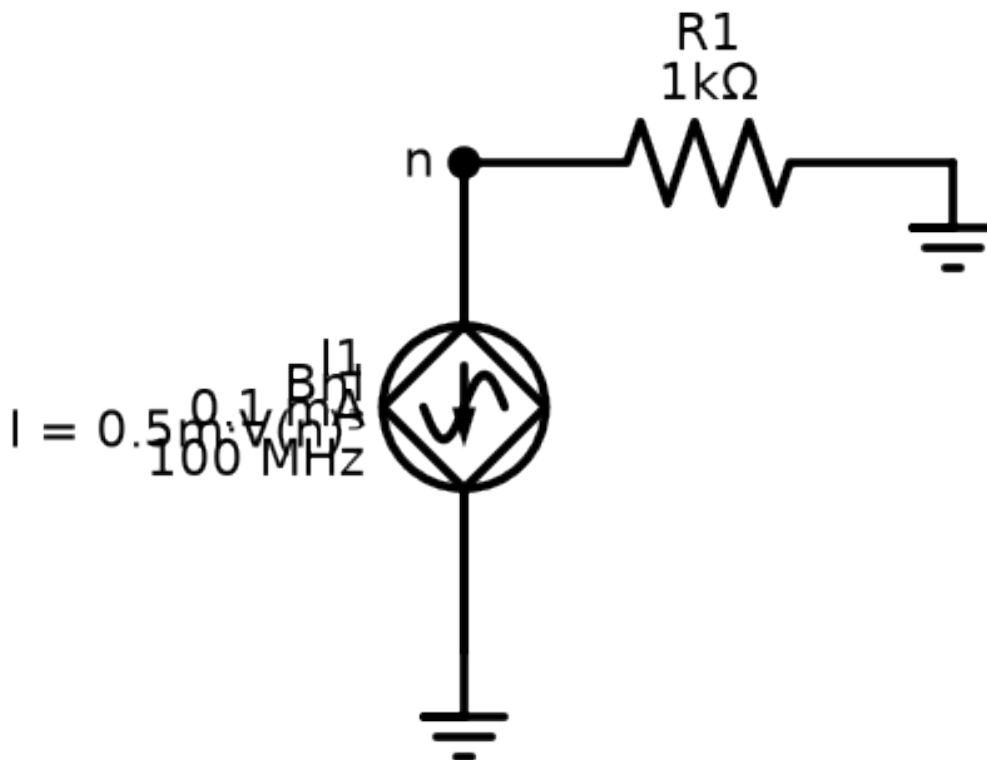Built-in — a cubic nonlinearity. A behavioral current source $I = 0.5m \cdot V^3$ is a clean, textbook nonlinearity:



```
* Harmonic balance of a cubic nonlinearity (built-in)
I1 0 n SIN(0 0.1m 100meg)
R1 n 0 1k
Bn1 n 0 I = 0.5e-3*V(n)*V(n)*V(n)
.options numdgt=8
.control
hb 100meg 6      $ fundamental 100 MHz, keep 6 harmonics
.endc
.end
```

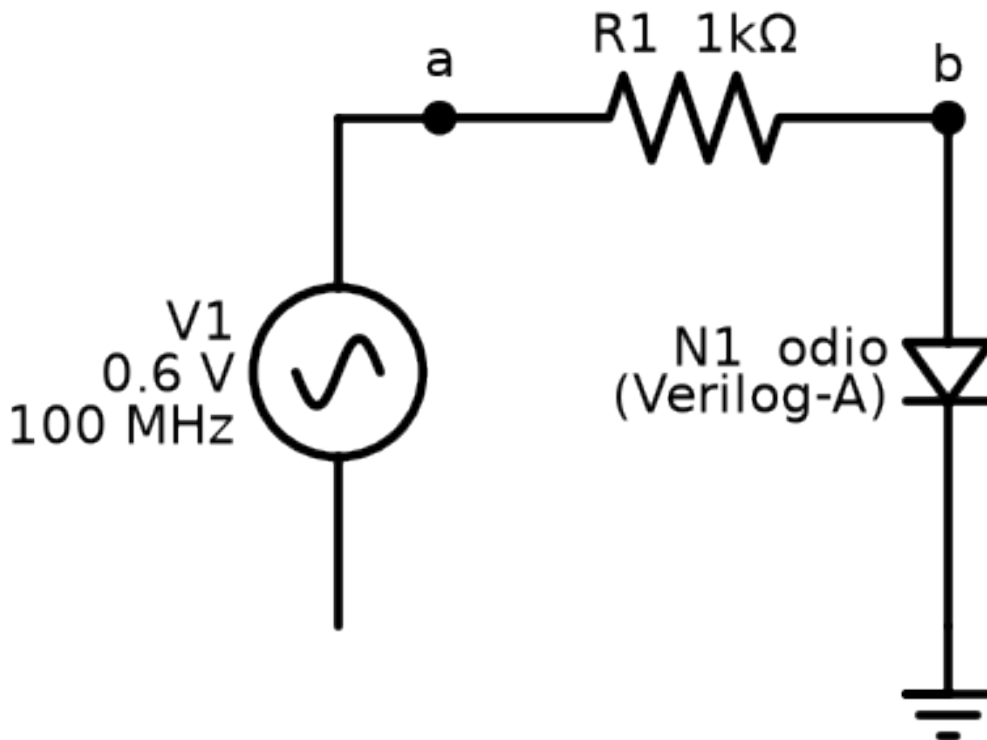OSDI — a Verilog-A diode. Same command, a compiled compact model as the nonlinearity:




* Harmonic balance of an OSDI diode

```
.control
pre_osdi rf_blocks.osdi
.endc
V1 a 0 SIN(0 0.6 100meg)
R1 a b 1k
N1 b 0 dd
.model dd odio is_=1e-14
.control
pre_osdi rf_blocks.osdi
hb 100meg 6
.endc
.end
```

The result.

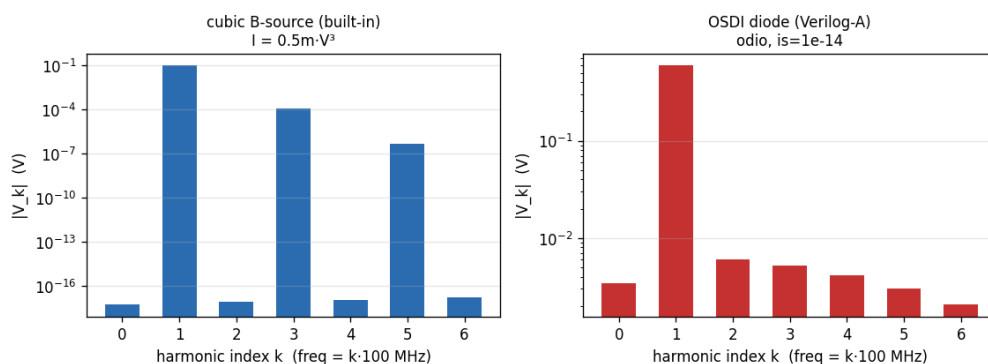Harmonic Balance (hb): steady-state harmonic spectrum



Why it is physically correct. The two nonlinearities have different *symmetry*, and the spectra show it:

- The cubic V^3 is an *odd* function. Feeding it a sine produces only odd harmonics (fundamental, 3rd, 5th, ...): $\sin^3 = \frac{3}{4} \cdot \sin - \frac{1}{4} \cdot \sin(3 \cdot)$. The even harmonics sit at the numerical floor — exactly

what an odd nonlinearity must do.


- The diode $\exp(V/V_T)$ has no symmetry, so it generates a full harmonic series (2nd, 3rd, 4th ... all present), plus a DC shift (rectification). This is why diodes make good mixers and detectors and cubic distortion does not.

Harmonic balance recovers both spectra from a single frequency-domain solve, with no time-stepping or FFT.

Part 3 — Periodic AC: conversion gain (**.pac**)


The idea. Once you have a periodic operating state (from PSS), you can ask the **.ac**-style question *around it*: inject a small signal at some frequency f_{in} and see how it comes out — not only at f_{in} , but at every sideband $f_{in} + k \cdot f_0$, because the pumped, time-varying circuit mixes the small signal up and down. That is exactly how a mixer's *conversion gain* is defined. **.pac** was built across [Enhancements 119–123](#): retain the PSS operating point, extract the periodic Jacobian's harmonics, assemble the $(2M+1)N$ harmonic conversion matrix, and solve it at each input frequency.

A correctness anchor everyone can check. For a *linear* circuit there is no mixing: the conversion matrix is block-diagonal, and the sideband-0 response is just the ordinary AC response. So **.pac** on our RC low-pass must reproduce the textbook driving-point impedance $|Z(f)| = 1 / |1/R + j\omega C|$. That is a strong, exact test that the whole PSS → conversion-matrix machinery is right.

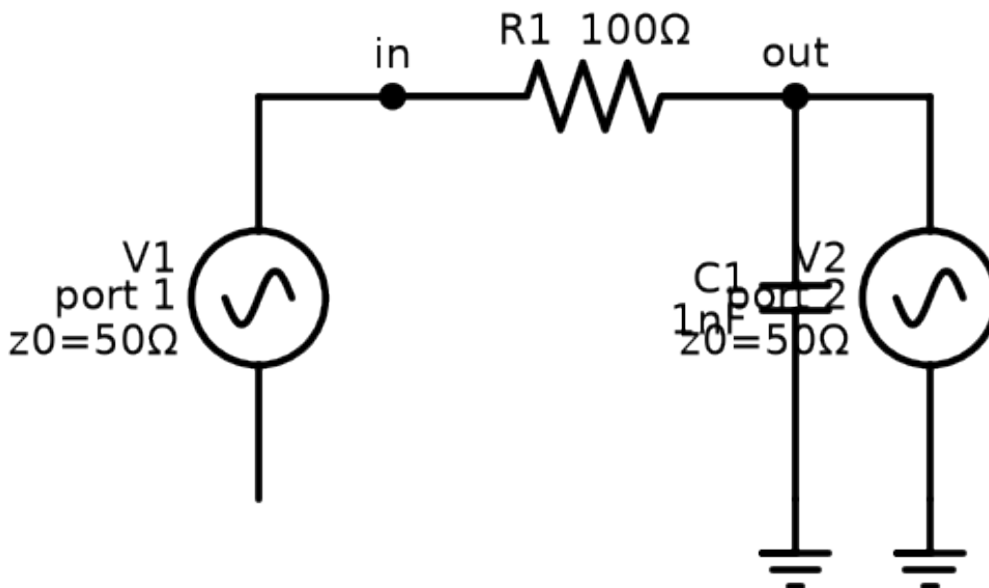

```
* Periodic AC of a driven RC low-pass
V1 a 0 SIN(0 1 1meg)
R1 a b 1k
C1 b 0 1n
* .pac <pss params> <dec|oct|lin> Npts Fstart Fstop [sideband]
.pac 1meg 1u b 512 8 40 5u dec 15 10k 10meg
.control
run
plot mag(b)
.endc
.end
```

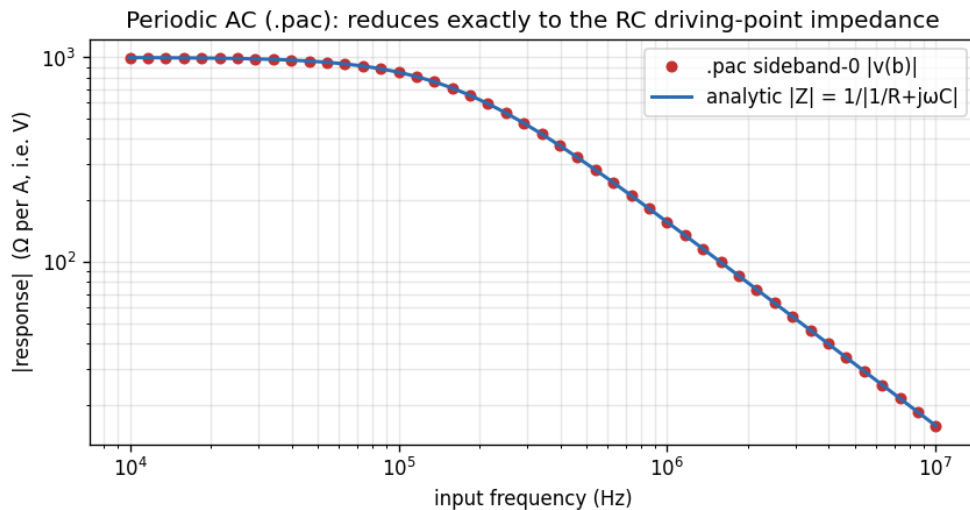The result — the **.pac** sideband-0 points fall exactly on the analytic RC impedance:



Why it is physically correct. The curve is flat at $R = 1 \text{ k}\Omega$ below the corner (the capacitor is open, so the node sees the full resistor) and rolls off at 20 dB/decade above $1/(2\pi RC) \approx 159 \text{ kHz}$ (the capacitor shorts the node). The simulated `.pac` markers land on the analytic $|Z|$ to plotting precision — the periodic small-signal solve reduces *exactly* to `.ac` when there is nothing to mix, which is precisely the guarantee you want before trusting it on a real mixer, where the conversion sidebands are nonzero and carry the interesting conversion-gain and image-rejection information.


Part 4 — Periodic noise (`.pnoise`)

The idea. Noise in a pumped circuit is subtler than ordinary `.noise`. A device's noise (thermal, shot, flicker) is itself modulated by the large periodic signal swinging its bias, and noise from every sideband folds down onto your output band. `.pnoise` ([Enhancement-124](#)) folds each device's noise through the *adjoint* of the same conversion matrix; the cyclostationary mode ([E-126](#), keyword `cyclo`) additionally tracks how the noise power breathes over the period.

Again a linear circuit gives an exact anchor: with no mixing, `.pnoise` must reduce to ordinary `.noise`. For our RC, only the resistor's thermal noise contributes, shaped by the low-pass — the classic result for the output-noise power spectral density $S_v(f) = 4kTR / (1 + (2\pi fRC)^2)$ (in V^2/Hz).

```
* Periodic noise of a driven RC low-pass
V1 a 0 DC 0 AC 1 SIN(0 1 1meg)
R1 a b 1k
C1 b 0 1n
* .pnoise <pss params> OutNode InSrc <dec|oct|lin> Npts Fstart Fstop [cyclo]
.pnoise 1meg 1u b 512 8 40 5u b v1 dec 15 10k 10meg
.control
run
plot onoise_spectrum
.endc
.end
```

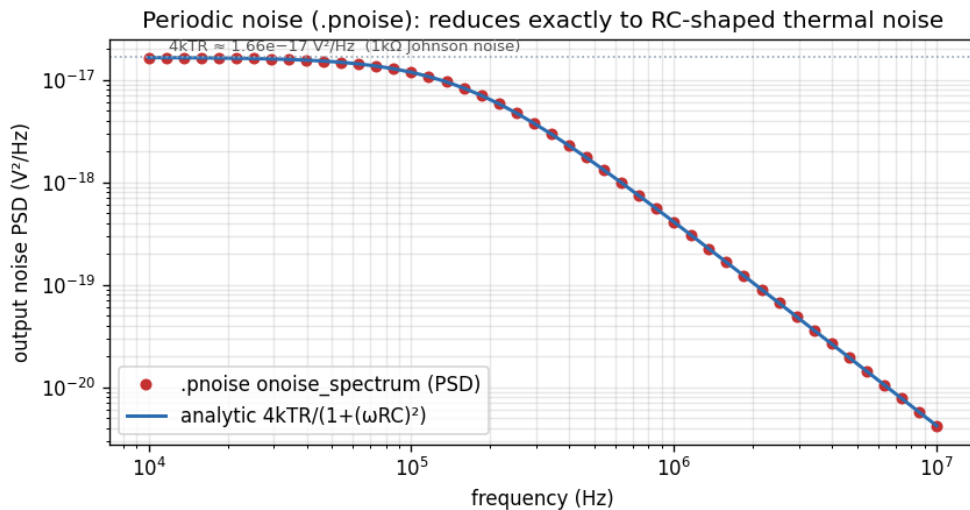The result — the `.pnoise` output-noise PSD matches $4kTR/(1+(\omega RC)^2)$:



Why it is physically correct. At low frequency the PSD is flat at $4kTR = 4 \cdot 1.38e-23 \cdot 300 \cdot 1000 \approx 1.66e-17 \text{ V}^2/\text{Hz}$ — the Johnson–Nyquist thermal noise of a $1\text{-k}\Omega$ resistor (equivalently $\sqrt{4kTR} \approx 4.1 \text{ nV}/\sqrt{\text{Hz}}$ as a density). Above the RC corner it rolls off with the same low-pass shape that filters the signal (the capacitor shorts high-frequency noise to ground just as it shorts the signal). The .pnoise markers sit on the analytic curve, confirming that the noise-folding machinery reduces to textbook thermal noise in the no-mixing limit — the prerequisite for trusting it on a real mixer, where it computes the noise figure that a plain .noise cannot see.


Part 5 — Periodic transfer function (.pxf) and S-parameters (.psp)

These two complete the periodic small-signal set and share the same conversion-matrix engine, so we present them compactly.

.pxf ([Enhancement-125](#)) is the *adjoint* of .pac: instead of “one input → all outputs”, it computes “all inputs → one output” — the transfer function from every sideband to a chosen node. By reciprocity its sideband-0 result is bit-identical to the .pac response, which is exactly how it is validated.

```
* Periodic transfer function to node b
V1 a 0 SIN(0 1 1meg)
R1 a b 1k
C1 b 0 1n
.pxf 1meg 1u b 512 8 40 5u b dec 15 10k 10meg 0
.control
run
plot mag(xf)
.endc
.end
```

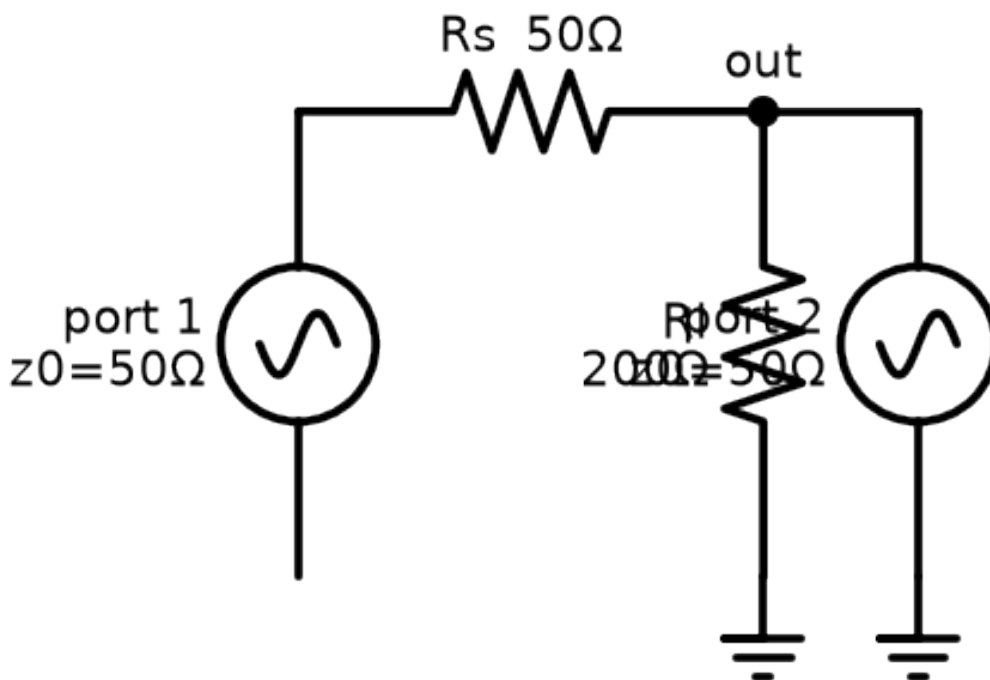.psp ([Enhancement-132](#)) computes periodic small-signal S-parameters: S-parameters of a circuit that is being pumped, so that they can differ from sideband to sideband (a time-varying network). For a time-invariant network they reduce exactly to ordinary .sp, the check used here on a resistive 2-port:




* Periodic S-parameters of a resistive 2-port (reduces to .sp)

```
V1 in 0 DC 0 AC 1 portnum 1 z0 50
V2 out 0 DC 0 AC 1 portnum 2 z0 50
Rs in out 50
Rl out 0 200
Rp out 0 200
Vpss pssref 0 SIN(0 0.01 100meg)
Rpss pssref 0 1k
.psp 100meg 1u pssref 256 4 20 5u lin 1 100meg 100meg
.control
run
print s_1_1 s_2_1 s_1_2 s_2_2
.endc
.end
```

For this resistive divider the sideband-0 S-parameters equal the analytic values of the 50-Ω/200-Ω network to $\sim 10^{-16}$, and the conversion sidebands are zero (a linear network does not mix) — the signature that the machinery is correct.

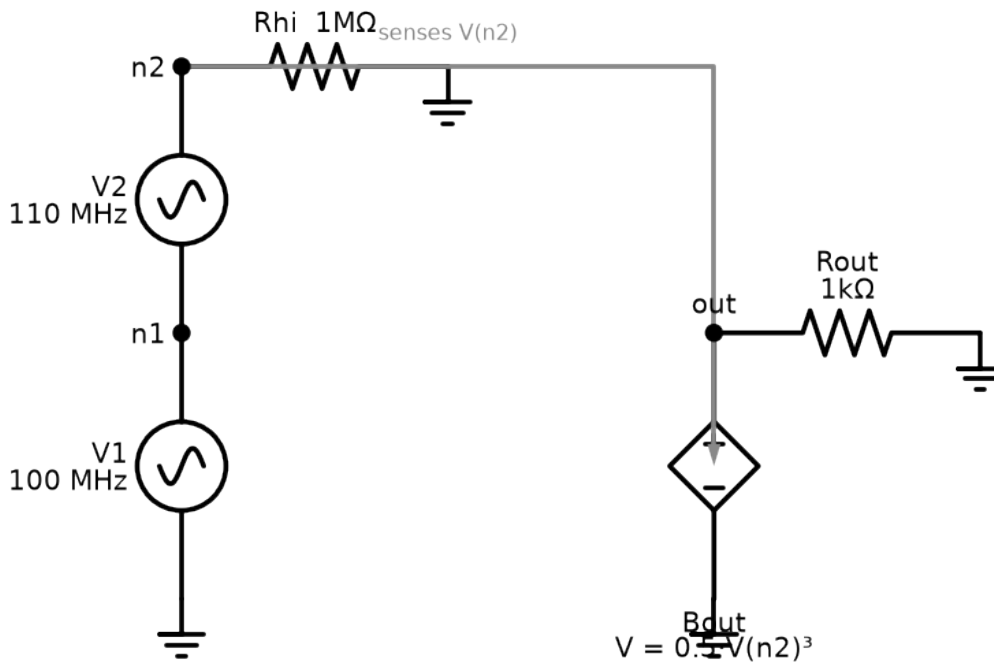Part 6 — Two tones at once: quasi-periodic steady state (**qpss**)

The idea. Real RF systems handle two signals whose frequencies are not simple multiples of each other — a wanted signal and an interferer, or two carriers in a power amplifier. Their mixing products live on a 2-D grid $k_1 \cdot f_1 + k_2 \cdot f_2$. The nastiest are the third-order intermodulation (IM3) products $2f_1 - f_2$ and $2f_2 - f_1$, because they land *right next* to the wanted tones and cannot be filtered out. qpss ([Enhancement-133](#), [-136](#)) computes this two-tone spectrum directly. The small-signal qpac/qpnoise/qpxf ([E-137–142](#)) mirror the single-tone trio around this two-tone state.



* Two-tone QPSS through a cubic nonlinearity

V1 n1 0 SIN(0 0.1 100meg)

V2 n2 n1 SIN(0 0.1 110meg)

Rhi n2 0 1meg

Bout out 0 V = 0.5*V(n2)*V(n2)*V(n2)

Rout out 0 1k


.control

qpss v(out) 100meg 110meg 4 3 \$ tones 100 & 110 MHz, up to order 4, 3 harmonics

.endc

.end

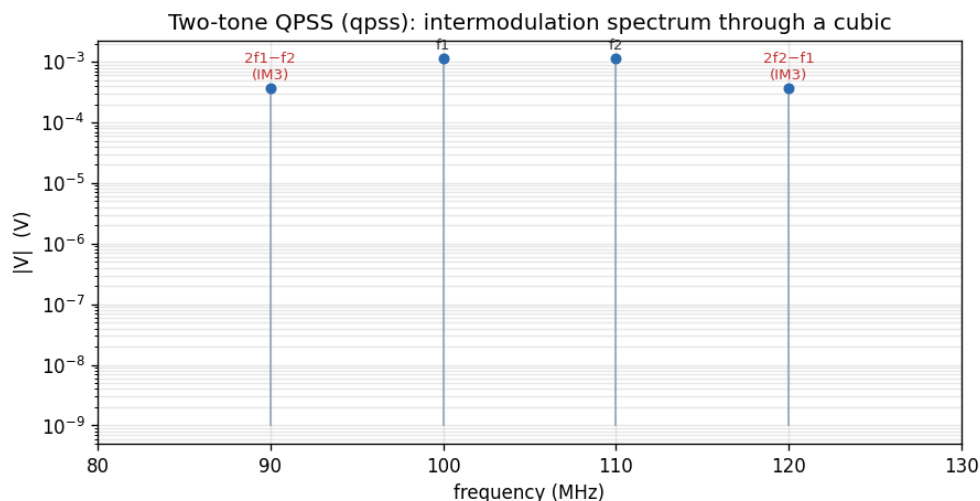
The result — the two big tones at 100 and 110 MHz, flanked by the IM3 products at 90 and 120 MHz:



Why it is physically correct. A cubic V^3 acting on $\cos(\omega_1 t) + \cos(\omega_2 t)$ produces, among its terms, $2\omega_1 - \omega_2$ and $2\omega_2 - \omega_1$ — the IM3 products — at 90 MHz and 120 MHz, symmetric about the two tones. Their amplitude grows as the cube of the drive (the famous 3-dB-per-dB, "3:1 slope" that defines a circuit's third-order intercept point, IP3). qpss places them at exactly the right frequencies with the right relative size, which is why it is the workhorse for linearity/IP3 characterisation.

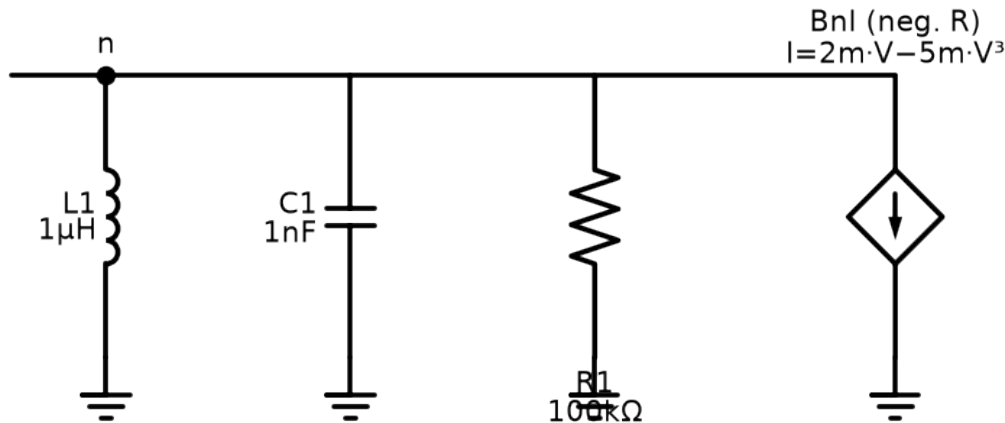Part 7 — Oscillators: **hbosc** + **phasennoise**

The idea. An oscillator has no input tone — it generates its own. Simulating it is special: you must solve for the unknown oscillation frequency at the same time as the waveform. **hbosc** ([Enhancement-140](#)) does this with an *autonomous* harmonic balance (a bordered Newton that treats ω_0 as an extra unknown). Once the limit cycle is known, **phasennoise** computes the phase-noise spectrum $L(\Delta f)$ — how much the oscillator's phase jitters, the single most important spec of any RF oscillator or clock.



* LC oscillator: tank + cubic negative resistance

L1 n 0 1u

C1 n 0 1n

Bn1 0 n I = 2m*V(n) - 5m*V(n)*V(n)*V(n) \$ negative resistance sustains oscillation

R1 n 0 100k

.ic V(n)=0.1

.control


hbosc n 5 5.0329meg 60u \$ find the limit cycle: node n, 5 harmonics, ~5.03 MHz guess

phasennoise 1k 10meg 5 \$ phase noise from 1 kHz to 10 MHz offset

.endc

.end

The result — the phase-noise skirt:

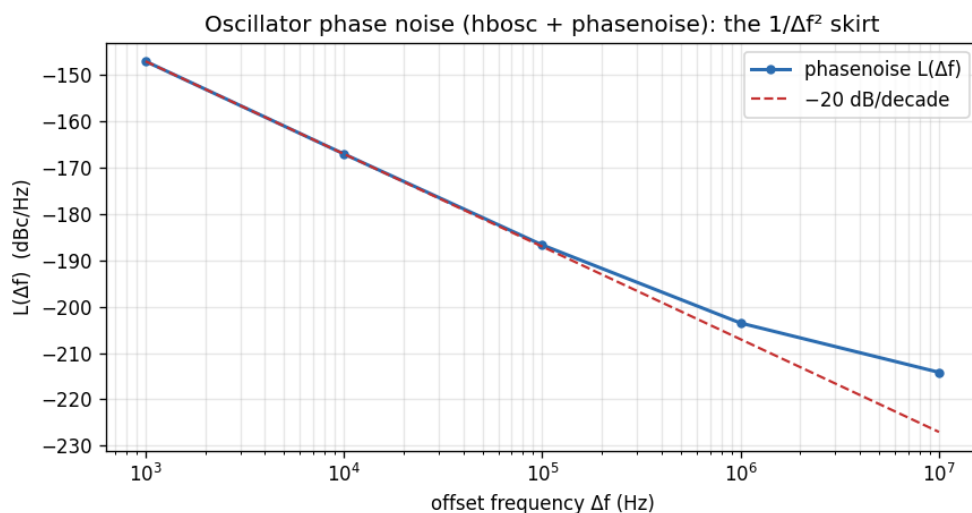


Why it is physically correct. The tank resonates at $f_0 = 1/(2\pi\sqrt{LC}) = 1/(2\pi\sqrt{1\mu\text{H}\cdot 1\text{nF}}) \approx 5$.

03 MHz, and hosc converges to exactly that frequency and the amplitude set by the cubic's negative resistance balancing the tank loss. The phase-noise curve falls at -20 dB/decade close to the carrier: thermal noise perturbs the oscillator's phase, and because nothing restores absolute phase (the oscillator is free-running), that phase noise integrates into a $1/\Delta f^2$ power law — the universal near-carrier signature of an LC oscillator. Far from the carrier it flattens toward the noise floor. Both regions appear in the plot.

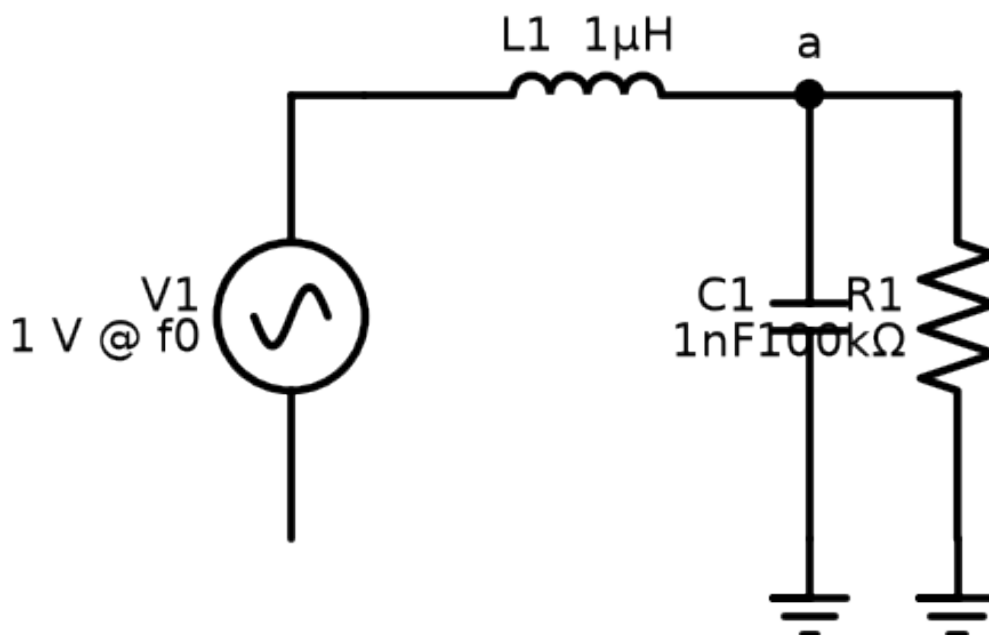
Part 8 — Envelope following (**envelope**)

The idea. Sometimes a fast carrier has a slowly varying envelope — a resonator ringing up over thousands of cycles, a PLL settling, a modulated power amplifier. A plain `.tran` must grind through every fast cycle. Envelope following ([Enhancement-154](#)) samples the state once per carrier period and integrates the *slow* drift of those samples, jumping many periods at a time — with an implicit step so it stays stable even on high-Q resonators (where the naive explicit jump blows up).



```
* Envelope following: high-Q RLC tank rung up by an on-resonance carrier
v1 s 0 sin(0 1 5.032921e6)
l1 s a 1u
c1 a 0 1n
r1 a 0 100k
.control
envelope a 5.032921e6 596u
plot a_amp          $ the amplitude envelope versus (slow) time
.endc
.end
```

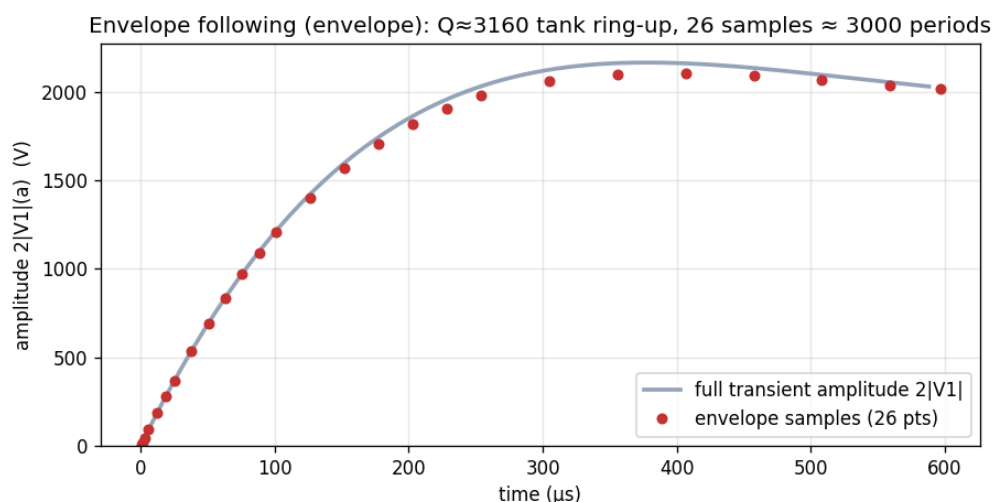The result — 26 envelope samples reproduce a 3000-cycle ring-up:



Why it is physically correct. With $R = 100 \text{ k}\Omega$ the tank's quality factor is $Q = R \cdot \sqrt{C/L} \approx 3160$, so it rings up to its steady amplitude over roughly $Q/\pi \approx 1000$ carrier periods — a textbook exponential approach. The envelope samples trace exactly that ring-up (they lie on the amplitude curve extracted from a full transient), while using a few dozen period-solves instead of thousands of time steps. The method converges to the correct steady amplitude and never diverges — the payoff of the implicit, monodromy-based step.

Part 8b — Design aids built on the same machinery

Three commands reuse the S-parameter and PSS engines rather than adding new numerics of their own.

stb — loop-gain and stability margins (E-198). Middlebrook/Tian double injection: a series voltage probe and a shunt current probe are inserted at one break in the feedback path, and the loop gain is recovered from both injections. The double form is what makes a *loaded* break correct — a single injection mis-measures the loop whenever the driving stage has finite output impedance. Reports phase and gain margin with the crossing frequencies, and leaves `loopgain` as a complex vector.

rfstab — two-port RF stability (E-253). From the S-parameters already computed by `sp`: Rollett's K with $|\Delta|$, the geometric μ and μ' factors, and MSG/MAG. Reports the worst case over the sweep and whether the network is unconditionally stable everywhere ($K > 1$ and $|\Delta| < 1$).

loadpull — PA load- and source-pull (E-234). Sweeps the load reflection coefficient Γ across the Smith chart, running a large-signal analysis per point and contouring delivered power and efficiency; `-source` does the source-side sweep. Finding a real use-after-free in `INPretrieve` while building this is what exposed the `INPretrieve(&x); ... tfree(x)` double-free class later fixed in `stb` too (E-235).

Part 9 — It all works under both linear solvers

Every analysis above is independent of the linear solver. ngspice ships with two: the default Sparse 1.3 and the optional KLU (`.option klu`). The RF engines each carry out their own dense conversion-matrix / harmonic-balance solve and only *read* the device Jacobian off the matrix, so the choice of solver does not change the answer. PSS, HB, PSP, QPSS, and envelope following are verified bit-identical under both (E-118, -132, -134, -136). The one caveat is speed: the shooting-PSS analyses (`.pss/.pac/.pnoise/.pxf/.psp`) force a full re-factor each shooting step, so they run noticeably slower under KLU — a performance trade, not a correctness one.

Summary

You want to know...	Use	Built-in example	OSDI example
filter/match response vs. frequency	<code>.sp</code>	RC low-pass	RC low-pass (ores+ocap)
the repeating large-signal waveform	<code>.pss / hb</code>	cubic nonlinearity	odio diode
small-signal gain / conversion	<code>.pac</code>	RC ($\rightarrow$ AC impedance)	—
noise of a pumped circuit	<code>.pnoise</code>	RC ($\rightarrow$ thermal noise)	—
transfer / S-params of a pumped net	<code>.pxf / .psp</code>	RC / resistive 2-port	—
two-tone intermodulation (IP3)	<code>qpss</code>	cubic $\rightarrow$ IM3	—
an oscillator's frequency + jitter	<code>hbosc + phasenoise</code>	LC oscillator	—
the slow envelope of a fast carrier	<code>envelope</code>	high-Q RLC tank	—

The RF/periodic-steady-state suite is, to our knowledge, the most complete such suite in any open-source SPICE — and it treats compiled built-in devices and Verilog-A/OSDI compact models identically throughout. For the full implementation story of any analysis, follow its enhancement link above; for where it sits relative to commercial tools, see the [gap analysis](#).

All schematics: [make_rf_schematics.py](#). All result plots: [make_rf_figs.py](#), generated from real runs of the committed `ngspice`.